

Reg No.: _____

Name: _____


APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S8 (R,S) Exam April 2025 (2019 Scheme)


Course Code: ECT466**Course Name: ANALOG CMOS DESIGN****Max. Marks: 100****Duration: 3 Hours****PART A***Answer all questions, each carries 3 marks.*

Marks


- 1 Comment on sub threshold conduction in MOSFETs. (3)
- 2 Draw the circuit for CS amplifier with current source load and diode connected load. (3)
- 3 Draw the transfer characteristics of differential output versus differential input voltage ($\Delta V_{in} = V_{in1} - V_{in2}$) for a resistive loaded differential amplifier. (3)
- 4 What is the main issue with the differential amplifier shown below? (3)

 

 
- 5 Draw the high frequency small signal model of the common source amplifier shown below. (3)



 - 6 Find the input pole of the amplifier using miller approximation (3)



 - 7 Explain flicker noise in a MOSFET and find the noise current due to it in the output circuit. (3)
- 8 Find the total thermal output noise power per bandwidth of the common source amplifier. (3)



- 9 Draw and explain the block diagram of a simple PLL (3)
- 10 What is the advantage of using PFD over a PD in a PLL ? (3)

PART B


Answer any one full question from each module, each carries 14 marks.

Module I

- 11 a) Comment in detail the large signal operation of the CS amplifier with resistive load. (8)
- b) Using small signal analysis find the voltage gain of the above circuit ($\lambda \neq 0$). (6)

OR


- 12 a) Derive the expression for voltage gain of a source follower. (7)
- b) Find the output resistance (R_{out}) for the circuit diagram shown below. (7)

 

Module II


- 13 a) Derive the expression of small signal voltage gain of differential amplifier shown. (8)

 Assume $g_{m1}=g_{m2}=g_{mN}$ and $g_{m3}=g_{m4}=g_{mP}$.



 
- b) Find the drain current of M_4 if all of the transistors are in saturation. $I_{REF} = 50\mu A$. (6)

$(W/L)_2=5 (W/L)_1$ and $(W/L)_4 =4 (W/L)_3$



OR

 - 14 a) Derive the common mode and differential mode gain for the circuit shown below. (10)



- b) Comment on the advantages of cascode current mirror over simple current mirror circuits. (4)

Module III


- 15 a) Draw the high frequency equivalent circuit of source follower and find the voltage transfer function. (14)

OR

- 16 a) Explain Miller theorem. (4)
 b) Using approximate high frequency model find the poles in a Common Source amplifier. (10)

Module IV

 - 17 a) Calculate the output noise power per unit bandwidth and input-referred $1/f$ and thermal noise voltage of the CS stage depicted below, assuming M_1 and M_2 are in saturation ($\lambda=0$). Trans conductance of MOSFETs are g_{m1} , g_{m2} and dimensions of MOSFETs are $(W/L)_1$ and $(W/L)_2$ (14)



OR

- 18 a) For an NMOS current source, calculate the total thermal and $1/f$ noise in the drain (8)

current for a band from 1KHz to 1MHz .

- b) Explain the noise analysis procedure to find the total noise at the output due to various noise sources in a circuit. (6)

Module V

- 19 a) Derive the open loop and closed loop transfer function of a type 1 PLL. (8)
b) How is skew reduction possible using PLL? (6)

OR

- 20 a) With the help of diagrams, explain the working of a charge-pump (type-2) PLL. Derive expression for the transfer function. (14)
