

Course Code: EET292

Course Name: NETWORK ANALYSIS AND SYNTHESIS

Max. Marks: 100

Duration: 3 Hours

**PART A***(Answer all questions; each question carries 3 marks)*

Marks


- |    |  |   |
|----|--|---|
| 1  | What are the properties of incidence matrix associated with graph theory?                    | 3 |
| 2  | Explain the following terms i) Tree ii) Oriented graph iii) Twig                             | 3 |
| 3  | Obtain the relationship between branch current matrix and loop current matrix.               | 3 |
| 4  | State and explain Tellegen's theorem.  | 3 |
| 5  | What is propagation constant? Obtain the propagation constant of $\pi$ network.              | 3 |
| 6  | What is constant k low pass filter? Obtain its frequency response.                           | 3 |
| 7  | Explain what is meant by poles and zeros of a network function?                              | 3 |
| 8  | List the properties of positive real functions   | 3 |
| 9  | What are the properties of LC immittance functions   | 3 |
| 10 | What is the network interpretation of removal of a pole at origin for an impedance function? | 3 |

**PART B***(Answer one full question from each module, each question carries 14 marks)***Module -1**


- 11 a) The reduced incidence matrix of an oriented graph is given below. Draw the graph. 7

$$A = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

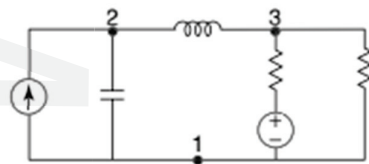- b) How many trees are possible for the graph of the network of Fig.? 7




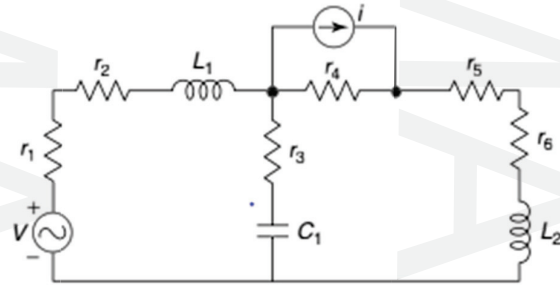- 12 i) State and express Kirchoff's Voltage law in topological form 14  
 ii) For the circuit shown in Fig. Draw the oriented graph and write (a) incidence Matrix (b) tie set matrix




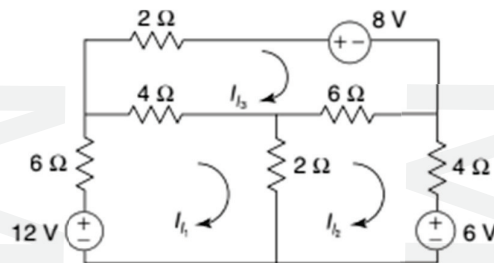**Module -2**

- 13 For the network shown in Fig. , write down the tie set matrix and obtain the network equilibrium equation in matrix form using KVL. Calculate loop currents. 14



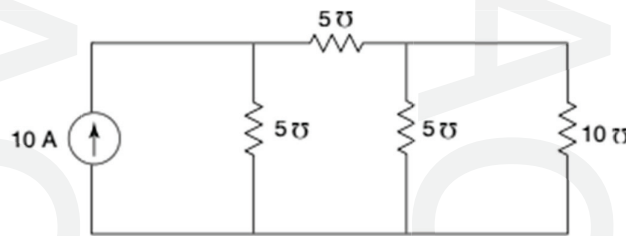- 14 For the network shown in Fig. obtain equilibrium equation on node basis. 14




**Module -3**

- 15 a) Obtain the characteristic impedance of a T network 8  
 b) The ABCD parameters of a network are given as  $A = \frac{6}{5}$ ,  $B = \frac{17}{5}$ ,  $C = \frac{1}{5}$  &  $D = \frac{7}{5}$  6  
 . Find the image parameters and propagation constant.  
 16 a) Design a constant -k high pass filter having cut off frequency of 1000Hz with 8  
 a load resistance of 600 Ω  
 b) Explain functionality of an attenuator and its various types? 6

Module -4

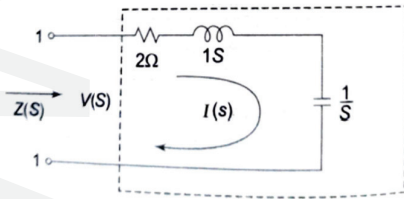- 17 a) Determine the driving point impedance of the network shown in figure and hence plot the poles and zeros in the s plane 8



- b) What are the transfer functions of a two port network? Explain. 6
- 18 a) Test whether the following polynomials are Hurwitz or not 6

i)  $S^4 + 7S^3 + 6S^2 + 21S + 8$

ii)  $S^5 + S^3 + S$

iii)  $S^4 + S^3 + 5S^2 + 3S + 4$

- b) Check whether the following functions are positive real or not. 8

i)  $F(s) = \frac{S^2 + S + 6}{S^2 + S + 1}$

ii)  $F(s) = \frac{S^3 + 6S^2 + 7S + 3}{S^2 + 2S + 1}$

Module -5

- 19 Realize following RL impedance function in Foster-I and Foster-II form. 14

$$\frac{Z(s)}{S} = \frac{(S + 1)(S + 4)}{S(S + 5)(S + 3)}$$

- 20 a) Realize the Cauer I and II form of the following LC function 10

$$Z(s) = \frac{4(S^2 + 1)(S^2 + 9)}{S(S^2 + 4)}$$

- b) Test whether the following functions are either RL RC or LC impedance functions 4

i)  $Z(s) = \frac{4(S+1)(S+3)}{S(S+2)}$

ii)  $Z(s) = \frac{2(S+1)(S+3)}{(S+2)(S+6)}$

\*\*\*\*\*