

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S8 (R,S) Exam April 2025 (2019 Scheme)

Course Code: EET466**Course Name: HVDC AND FACTS****Max. Marks: 100****Duration: 3 Hours****PART A***Answer all questions, each carries 3 marks.*

Marks

- | | | |
|----|---|-----|
| 1 | What is pulse number of a converter? What is its significance? | (3) |
| 2 | Differentiate between voltage sourced and current sourced converters. | (3) |
| 3 | Distinguish between delay in firing angle and extinction angle of an HVDC converter. | (3) |
| 4 | Discuss the current control strategy of the rectifier station in an HVDC transmission system. | (3) |
| 5 | What are the key differences between transient stability and steady-state stability in power systems? | (3) |
| 6 | What is power quality, and why is it important in electrical systems? | (3) |
| 7 | Explain different losses that are encountered with FC – TCR arrangement. | (3) |
| 8 | Explain the effect of initial charge of the capacitor in TSC. | (3) |
| 9 | Differentiate clearly between an UPFC & IPFC | (3) |
| 10 | State the objectives of voltage and phase angle regulators. | (3) |

PART B*Answer any one full question from each module, each carries 14 marks.***Module I**

- | | | |
|----|---|------|
| 11 | a) Derive the expression for average value of output voltage for a Graetz circuit with an overlap angle less than 60 degree | (10) |
| | b) State the merits of HVDC transmission over EHVAC transmission for bulk power transmission. | (4) |

OR

- | | | |
|----|--|-----|
| 12 | a) Explain voltage source converter with AC Current control with a neat control schematic. | (8) |
| | b) What are the different types of HVDC links? Discuss them with necessary diagrams. | (6) |

Module II

- 13 Explain the hierarchy of control in a detailed manner using a relevant block diagram. (14)

OR

- 14 a) Explain the static Vd-Id characteristics of HVDC system. Also explain the different modes of Rectifier and Inverter Station. (10)
b) Explain inverter extinction angle control. (4)

Module III

- 15 a) Derive the expression for active and reactive power for series compensation using a neat circuit diagram. (10)
b) Discuss various limitations on the loading of a transmission line. (4)

OR

- 16 a) Explain the effect of phase angle compensation with neat diagrams. (8)
b) What are the benefits of FACTS controllers? List different types of FACTS controllers? (6)

Module IV

- 17 a) Explain the working and characteristic of Thyristor Controlled Reactor. (8)
b) Differentiate between TSR and TCR. (6)

OR

- 18 a) Discuss the operation of STATCOM with a neat diagram and characteristics. (10)
b) What are the key advantages of a Static Synchronous Compensator? (4)

Module V

- 19 a) How an UPFC scheme can be implemented using two back to back voltage source converters. (10)
b) What are the key applications of a Unified Power Flow Controller (UPFC) in modern power systems? (4)

OR

- 20 a) Explain principle of operation of IPFC with neat diagram. Discuss its applications. (14)
